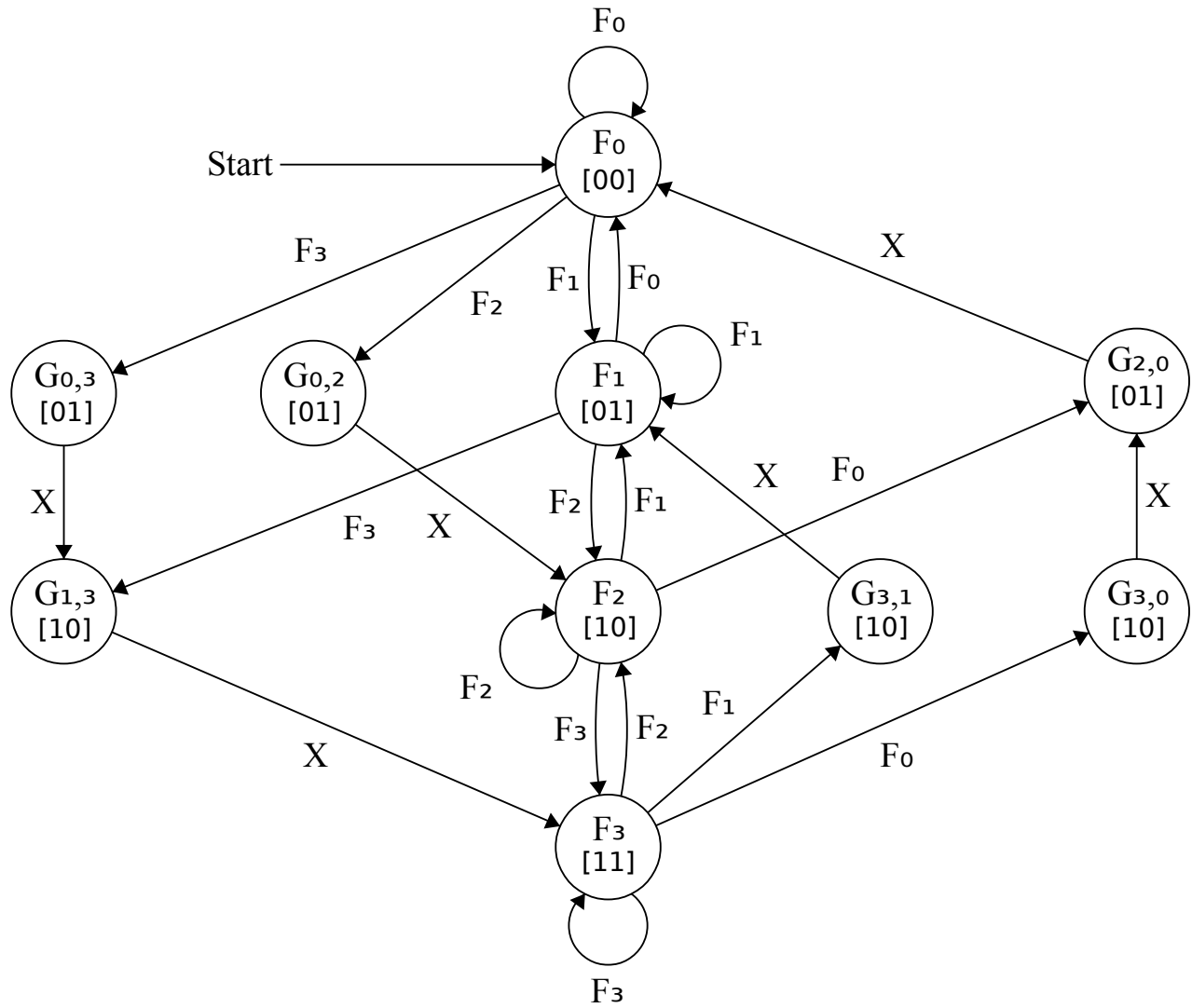


Moore FSM Diagram



States

$F_0 = 0000$

$F_1 = 0001$

$F_2 = 0010$

$F_3 = 0011$

$G_{0,2} = 0101$

$G_{1,3} = 0110$

$G_{2,0} = 1001$

$G_{3,1} = 1010$


$G_{0,3} = 1101$

$G_{3,0} = 1110$

State Transition Table

<u>Current State</u>				<u>Input</u>		<u>Next State</u>				<u>Output</u>	
Q ₃	Q ₂	Q ₁	Q ₀	B	A	Q ₃ ⁺	Q ₂ ⁺	Q ₁ ⁺	Q ₀ ⁺	Q ₁	Q ₀
0	0	0	0	0	0	0	0	0	0	0	0
				0	1	0	0	0	1	0	0
				1	0	0	1	0	1	0	0
				1	1	1	1	0	1	0	0
0	0	0	1	0	0	0	0	0	0	0	1
				0	1	0	0	0	1	0	1
				1	0	0	0	1	0	0	1
				1	1	0	1	1	0	0	1
0	0	1	0	0	0	1	0	0	1	1	0
				0	1	0	0	0	1	1	0
				1	0	0	0	1	0	1	0
				1	1	0	0	1	1	1	0
0	0	1	1	0	0	1	1	1	0	1	1
				0	1	1	0	1	0	1	1
				1	0	0	0	1	0	1	1
				1	1	0	0	1	1	1	1
0	1	0	1	X	X	0	0	1	0	0	1
0	1	1	0	X	X	0	0	1	1	1	0
1	0	0	1	X	X	0	0	0	0	0	1
1	0	1	0	X	X	0	0	0	1	1	0
1	1	0	1	X	X	0	1	1	0	0	1
1	1	1	0	X	X	1	0	0	1	1	0

Logisim Digital Circuit

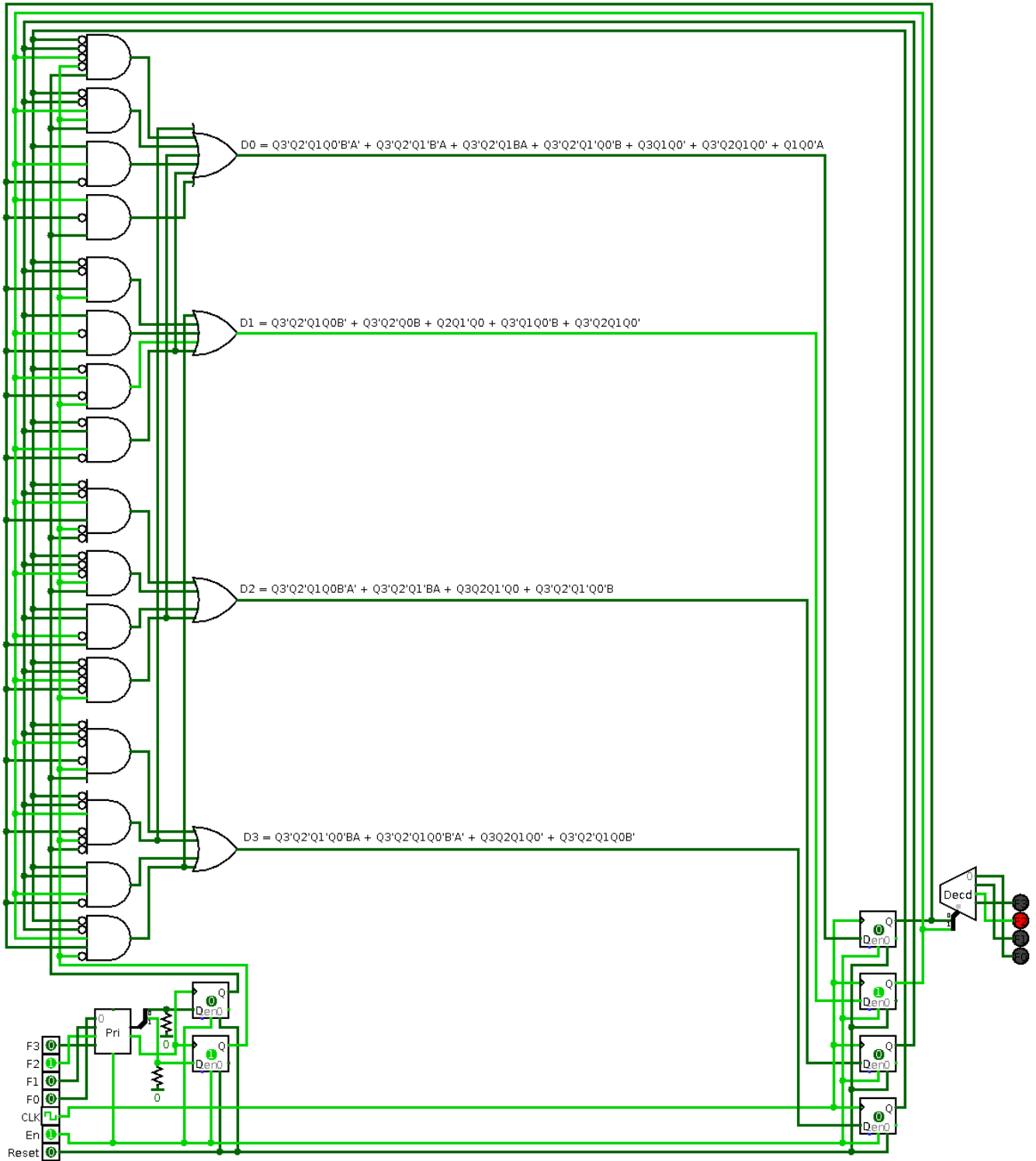

Python MyHDL Code

```
from myhdl import always, always_comb, always_seq, Signal, ResetSignal, toVerilog,
toVHDL, delay, traceSignals, Simulation, now, intbv, concat
```

#Implementation

```
def elevator(clk, reset, en, F, D, Q, A, B, A_latch, B_latch, LED):
```

```
    @always_comb
```

```
    def encoder():
```

```
        if bool(F) and en:
```

```
            A.next = bool(F[3] or (F[1] and not F[2]))
```

```
            B.next = bool(F[2] or F[3])
```

```
    @always_comb
```

```
    def latch():
```

```
        if reset:
```

```
            A_latch.next = bool(False)
```

```
            B_latch.next = bool(False)
```

```
        elif bool(F) and en:
```

```
            A_latch.next = A
```

```
            B_latch.next = B
```

```
    @always_comb
```

```
    def logic():
```

```
        D.next = concat(
            bool((not Q[3] and not Q[2] and not Q[1] and not Q[0] and
B_latch and A_latch) or (not Q[3] and not Q[2] and Q[1] and not Q[0] and not
B_latch and not A_latch) or (Q[3] and Q[2] and Q[1] and not Q[0]) or (not Q[3] and
not Q[2] and Q[1] and Q[0] and not B_latch)),
            bool((not Q[3] and not Q[2] and Q[1] and Q[0] and not
B_latch and not A_latch) or (not Q[3] and not Q[2] and not Q[1] and B_latch and
A_latch) or (Q[3] and Q[2] and not Q[1] and Q[0]) or (not Q[3] and not Q[2] and not
Q[1] and not Q[0] and B_latch)),
            bool((not Q[3] and not Q[2] and Q[1] and Q[0] and not
B_latch) or (not Q[3] and not Q[2] and Q[0] and B_latch) or (Q[2] and not Q[1] and
Q[0]) or (not Q[3] and Q[1] and not Q[0] and B_latch) or (not Q[3] and Q[2] and
Q[1] and not Q[0])),
            bool((not Q[3] and not Q[2] and Q[1] and not Q[0] and not
B_latch and not A_latch) or (not Q[3] and not Q[2] and not Q[1] and not B_latch and
A_latch) or (not Q[3] and not Q[2] and Q[1] and B_latch and A_latch) or (not Q[3]
and not Q[2] and not Q[1] and not Q[0] and B_latch) or (Q[3] and Q[1] and not Q[0])
or (not Q[3] and Q[2] and Q[1] and not Q[0]) or (Q[1] and not Q[0] and
A_latch))
        )
```

```
    @always_seq(clk.posedge, reset)
```

```
    def dff():
```

```
        if en:
```

```
            Q.next = D
```

```
    @always_comb
```

```
    def decoder():
```

```
        LED.next = concat(
            bool(Q[1] and Q[0]),
            bool(Q[1] and not Q[0]),
            bool(not Q[1] and Q[0]),
            bool(not Q[1] and not Q[0])
        )
```

```
    return encoder, latch, logic, dff, decoder
```

Python MyHDL to Verilog and VHDL Conversion Code

#Convert to Verilog

```
def convert():
    clk = Signal(bool(False))
    reset = ResetSignal(bool(False), bool(True), async=True)
    en = Signal(bool(True))
    F = Signal(intbv(0b0, 0b0, 0b10000))
    D = Signal(intbv(0b0, 0b0, 0b10000))
    Q = Signal(intbv(0b0, 0b0, 0b10000))
    A = Signal(bool(False))
    B = Signal(bool(False))
    A_latch = Signal(bool(False))
    B_latch = Signal(bool(False))
    LED = Signal(intbv(0b0, 0b0, 0b10000))
    toVerilog.timescale = "100ms/1ms"
    toVerilog(elevator, clk, reset, en, F, D, Q, A, B, A_latch, B_latch, LED)
    toVHDL(elevator, clk, reset, en, F, D, Q, A, B, A_latch, B_latch, LED)

convert()
```

Python MyHDL Simulation Code

```
#Simulate

def test_elevator():
    clk = Signal(bool(False))
    reset = ResetSignal(bool(False), bool(True), async=True)
    en = Signal(bool(True))
    F = Signal(intbv(0b0, 0b0, 0b10000))
    D = Signal(intbv(0b0, 0b0, 0b10000))
    Q = Signal(intbv(0b0, 0b0, 0b10000))
    A = Signal(bool(False))
    B = Signal(bool(False))
    A_latch = Signal(bool(False))
    B_latch = Signal(bool(False))
    LED = Signal(intbv(0b0, 0b0, 0b10000))
    elevator_inst = elevator(clk, reset, en, F, D, Q, A, B, A_latch, B_latch, LED)

@always(delay(10))
def clkgen():
    clk.next = not clk

@always(delay(1))
def stimulus():
    if now() == 45:
        F.next = Signal(intbv(0b0100))
    elif now() == 46:
        F.next = Signal(intbv(0b0000))
    elif now() == 60:
        F.next = Signal(intbv(0b0001))
    elif now() == 61:
        F.next = Signal(intbv(0b0000))
    elif now() == 150:
        F.next = Signal(intbv(0b0010))
    elif now() == 200:
        F.next = Signal(intbv(0b0011))
    elif now() == 250:
        F.next = Signal(intbv(0b0100))
    elif now() == 300:
        F.next = Signal(intbv(0b0101))
    elif now() == 350:
        F.next = Signal(intbv(0b0110))
    elif now() == 400:
        F.next = Signal(intbv(0b0111))
    elif now() == 450:
        F.next = Signal(intbv(0b1000))
    elif now() == 500:
        F.next = Signal(intbv(0b1001))
    elif now() == 550:
        F.next = Signal(intbv(0b1010))
    elif now() == 600:
        F.next = Signal(intbv(0b1011))
    elif now() == 650:
        F.next = Signal(intbv(0b1100))
        #reset.next = 0b1
    elif now() == 700:
        F.next = Signal(intbv(0b1101))
    elif now() == 750:
        F.next = Signal(intbv(0b1110))
    elif now() == 800:
        F.next = Signal(intbv(0b0001))
    elif now() == 850:
        F.next = Signal(intbv(0b1000))
        #reset.next = 0b0
    elif now() == 900:
        F.next = Signal(intbv(0b0010))
    elif now() == 950:
        F.next = Signal(intbv(0b1000))
        #en.next = 0b0
    elif now() == 1000:
        F.next = Signal(intbv(0b0001))
    elif now() == 1050:
        F.next = Signal(intbv(0b0100))
    elif now() == 1100:
        F.next = Signal(intbv(0b0001))
    elif now() == 1150:
        F.next = Signal(intbv(0b0100))
    elif now() == 1200:
        F.next = Signal(intbv(0b0000))
    elif now() == 1240:
        F.next = Signal(intbv(0b0000))
        #en.next = 0b1
    elif now() == 1360:
        F.next = Signal(intbv(0b0001))
    elif now() == 1370:
        F.next = Signal(intbv(0b1001))

    return elevator_inst, clkgen, stimulus#, reset_test, en_test

def simulate(timesteps):
    traceSignals.timescale = "100ms"
    tb = traceSignals(test_elevator)
    sim = Simulation(tb)
    sim.run(timesteps)

simulate(1500)
```

Verilog Code

```
// File: elevator.v
// Generated by MyHDL 0.8.1
// Date: Sun Jun 14 22:11:56 2015
```

```
`timescale 100ms/1ms

module elevator (
    clk,
    reset,
    en,
    F,
    D,
    Q,
    A,
    B,
    A_latch,
    B_latch,
    LED
);

input clk;
input reset;
input en;
input [3:0] F;
output [3:0] D;
wire [3:0] D;
output [3:0] Q;
reg [3:0] Q;
output A;
reg A;
output B;
reg B;
output A_latch;
reg A_latch;
output B_latch;
reg B_latch;
output [3:0] LED;
wire [3:0] LED;

always @(en, F) begin: ELEVATOR_ENCODER
    if (((F != 0) && en)) begin
        A = ((F[3] || (F[1] && (!F[2]))) != 0);
        B = ((F[2] || F[3]) != 0);
    end
end

always @(reset, A, B, en, F) begin: ELEVATOR_LATCH
    if (reset) begin
        A_latch = (1'b0 != 0);
        B_latch = (1'b0 != 0);
    end
    else if (((F != 0) && en)) begin
        A_latch = A;
        B_latch = B;
    end
end

assign D = {((((!Q[3]) && (!Q[2]) && (!Q[1]) && (!Q[0]) && B_latch && A_latch) || ((!Q[3]) && (!Q[2]) && Q[1] && (!Q[0]) && (!B_latch) && (!A_latch)) || (Q[3] && Q[2] && Q[1] && (!Q[0])) || ((!Q[3]) && (!Q[2]) && Q[1] && Q[0] && (!B_latch))) != 0), ((((!Q[3]) && (!Q[2]) && Q[1] && Q[0] && (!B_latch) && (!A_latch)) || ((!Q[3]) && (!Q[2]) && (!Q[1]) && (!Q[0]) && B_latch) && A_latch) || (Q[3] && Q[2] && (!Q[1]) && Q[0]) || ((!Q[3]) && (!Q[2]) && (!Q[1]) && (!Q[0]) && B_latch))) != 0), ((((!Q[3]) && (!Q[2]) && Q[1] && Q[0] && (!B_latch)) || ((!Q[3]) && (!Q[2]) && Q[0] && B_latch) || (Q[2] && (!Q[1]) && Q[0]) || ((!Q[3]) && Q[1] && (!Q[0]) && B_latch) || ((!Q[3]) && Q[2] && Q[1] && (!Q[0]))) != 0), ((((!Q[3]) && (!Q[2]) && Q[1] && (!Q[0]) && (!B_latch) && (!A_latch)) || ((!Q[3]) && (!Q[2]) && (!Q[1]) && (!B_latch) && A_latch) || ((!Q[3]) && (!Q[2]) && Q[1] && B_latch && A_latch) || ((!Q[3]) && (!Q[2]) && (!Q[1]) && (!Q[0]) && B_latch) || (Q[3] && Q[1] && (!Q[0])) || ((!Q[3]) && Q[2] && Q[1] && (!Q[0])) || (Q[1] && (!Q[0]) && A_latch)) != 0));

always @(posedge clk, posedge reset) begin: ELEVATOR_DFF
    if (reset == 1) begin
        Q <= 0;
    end
    else begin
        if (en) begin
            Q <= D;
        end
    end
end

assign LED = {((Q[1] && Q[0]) != 0), ((Q[1] && (!Q[0])) != 0), (((!Q[1]) && Q[0]) != 0), (((!Q[1]) && (!Q[0])) != 0)};

endmodule
```


VHDL Code

```
-- File: elevator.vhd
-- Generated by MyHDL 0.8.1
-- Date: Sun Jun 14 22:11:56 2015

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.numeric_std.all;
use std.textio.all;

use work.pck_myhdl_081.all;

entity elevator is
    port (
        clk: in std_logic;
        reset: in std_logic;
        en: in std_logic;
        F: in unsigned(3 downto 0);
        D: inout unsigned(3 downto 0);
        Q: inout unsigned(3 downto 0);
        A: inout std_logic;
        B: inout std_logic;
        A_latch: inout std_logic;
        B_latch: inout std_logic;
        LED: out unsigned(3 downto 0)
    );
end entity elevator;

architecture MyHDL of elevator is

begin

ELEVATOR_ENCODER: process (en, F) is
begin
    if (bool(F) and bool(en)) then
        A <= std1(bool(F(3)) or (bool(F(1)) and (not bool(F(2)))));
        B <= std1(bool(F(2)) or bool(F(3)));
    end if;
end process ELEVATOR_ENCODER;

ELEVATOR_LATCH: process (reset, A, B, en, F) is
begin
    if bool(reset) then
        A_latch <= '0';
        B_latch <= '0';
    elsif (bool(F) and bool(en)) then
        A_latch <= A;
        B_latch <= B;
    end if;
end process ELEVATOR_LATCH;

D <= unsigned('(((not bool(Q(3))) and (not bool(Q(2))) and (not bool(Q(1))) and (not bool(Q(0))) and bool(B_latch) and
bool(A_latch)) or ((not bool(Q(3))) and (not bool(Q(2))) and bool(Q(1)) and (not bool(Q(0))) and (not bool(B_latch)) and
(not bool(A_latch))) or (bool(Q(3)) and bool(Q(2)) and bool(Q(1)) and (not bool(Q(0))) or ((not bool(Q(3))) and (not
bool(Q(2))) and bool(Q(1)) and bool(Q(0)) and (not bool(B_latch))) & (((not bool(Q(3))) and (not bool(Q(2))) and
bool(Q(1)) and bool(Q(0)) and (not bool(B_latch)) and (not bool(A_latch))) or ((not bool(Q(3))) and (not bool(Q(2))) and
(not bool(Q(1))) and bool(B_latch) and bool(A_latch)) or (bool(Q(3)) and bool(Q(2)) and (not bool(Q(1))) and bool(Q(0)))
or ((not bool(Q(3))) and (not bool(Q(2))) and (not bool(Q(1))) and (not bool(Q(0))) and bool(B_latch))) & (((not
bool(Q(3))) and (not bool(Q(2))) and bool(Q(1)) and bool(Q(0)) and (not bool(B_latch))) or ((not bool(Q(3))) and (not
bool(Q(2))) and bool(Q(0)) and bool(Q(1)) and bool(B_latch)) or (bool(Q(2)) and (not bool(Q(1))) and bool(Q(0))) or ((not bool(Q(3)))
and bool(Q(1)) and (not bool(Q(0))) and bool(B_latch)) or ((not bool(Q(3))) and bool(Q(2)) and bool(Q(1)) and (not
bool(Q(0)))) & (((not bool(Q(3))) and (not bool(Q(2))) and bool(Q(1)) and (not bool(Q(0))) and (not bool(B_latch)) and
(not bool(A_latch))) or ((not bool(Q(3))) and (not bool(Q(2))) and (not bool(Q(1))) and (not bool(B_latch)) and
bool(A_latch)) or ((not bool(Q(3))) and (not bool(Q(2))) and bool(Q(1)) and bool(B_latch) and bool(A_latch)) or ((not
bool(Q(3))) and (not bool(Q(2))) and (not bool(Q(1))) and (not bool(Q(0))) and bool(B_latch)) or (bool(Q(3)) and
bool(Q(1)) and (not bool(Q(0)))) or ((not bool(Q(3))) and bool(Q(2)) and bool(Q(1)) and (not bool(Q(0))) or (bool(Q(1))
and (not bool(Q(0))) and bool(A_latch))));


ELEVATOR_DFF: process (clk, reset) is
begin
    if (reset = '1') then
        Q <= to_unsigned(0, 4);
    elsif rising_edge(clk) then
        if bool(en) then
            Q <= D;
        end if;
    end if;
end process ELEVATOR_DFF;

LED <= unsigned('((bool(Q(1)) and bool(Q(0))) & (bool(Q(1)) and (not bool(Q(0)))) & ((not bool(Q(1))) and bool(Q(0))) &
((not bool(Q(1))) and (not bool(Q(0)))));


end architecture MyHDL;
```

Waveform Viewer

Logic:

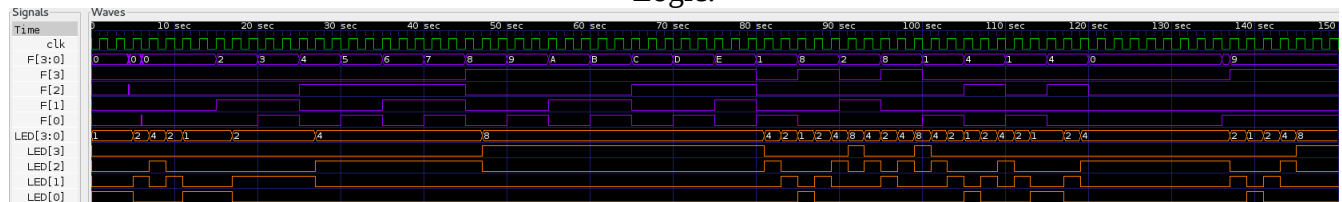

Reset and en:

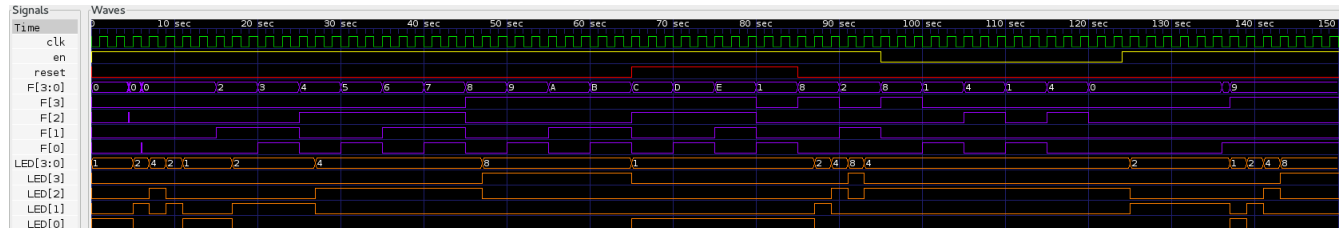

The design can be improved by having the output going back and forth between extremes when multiple buttons are selected simultaneously, optimally by first going to the closest floor. This can be implemented with an additional FSM in place of the priority encoder.